

1.1 Solution

Row	SOUT	CIN	$S = CIN \oplus SOUT$	$COOUT = CIN \cdot SOUT$
0	0	0	0	0
1	0	1	1	0
2	1	0	1	0
3	1	1	0	1

1.2 Solution


Cycle	RST	CIN	SOUT (at start of cycle)	$S = CIN \oplus SOUT$	$COUT = CIN \cdot SOUT$	$D = NAND(S, RS \cdot T)$	Notes / Truth-table row hit
0	0	0	X (unkno wn)	–	–	1	Init: force next SOUT=0
1	1	0	0	0	0	1	Row 0: (SOUT=0, CIN=0)
2	1	1	0	1	0	0	Row 1: (SOUT=0, CIN=1) → next SOUT=1
3	1	0	1	1	0	0	Row 2: (SOUT=1, CIN=0) → next SOUT=1
4	1	1	1	0	1	1	Row 3: (SOUT=1, CIN=1) → next SOUT=0

1.3 Solution


Per instructions, **annotate the first cycle** that exercises each truth-table row:

- Row 0 → **Cycle 1**
- Row 1 → **Cycle 2**
- Row 2 → **Cycle 3**
- Row 3 → **Cycle 4**


2.1 Solution

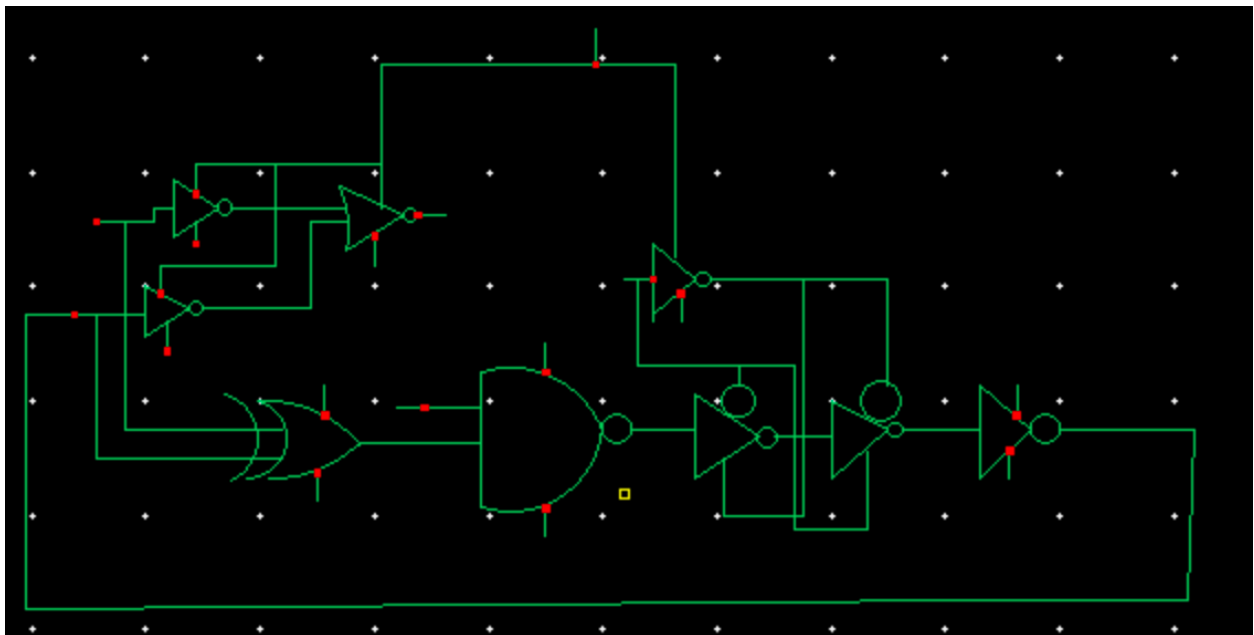


2.2 Solution

 


NOT GATE

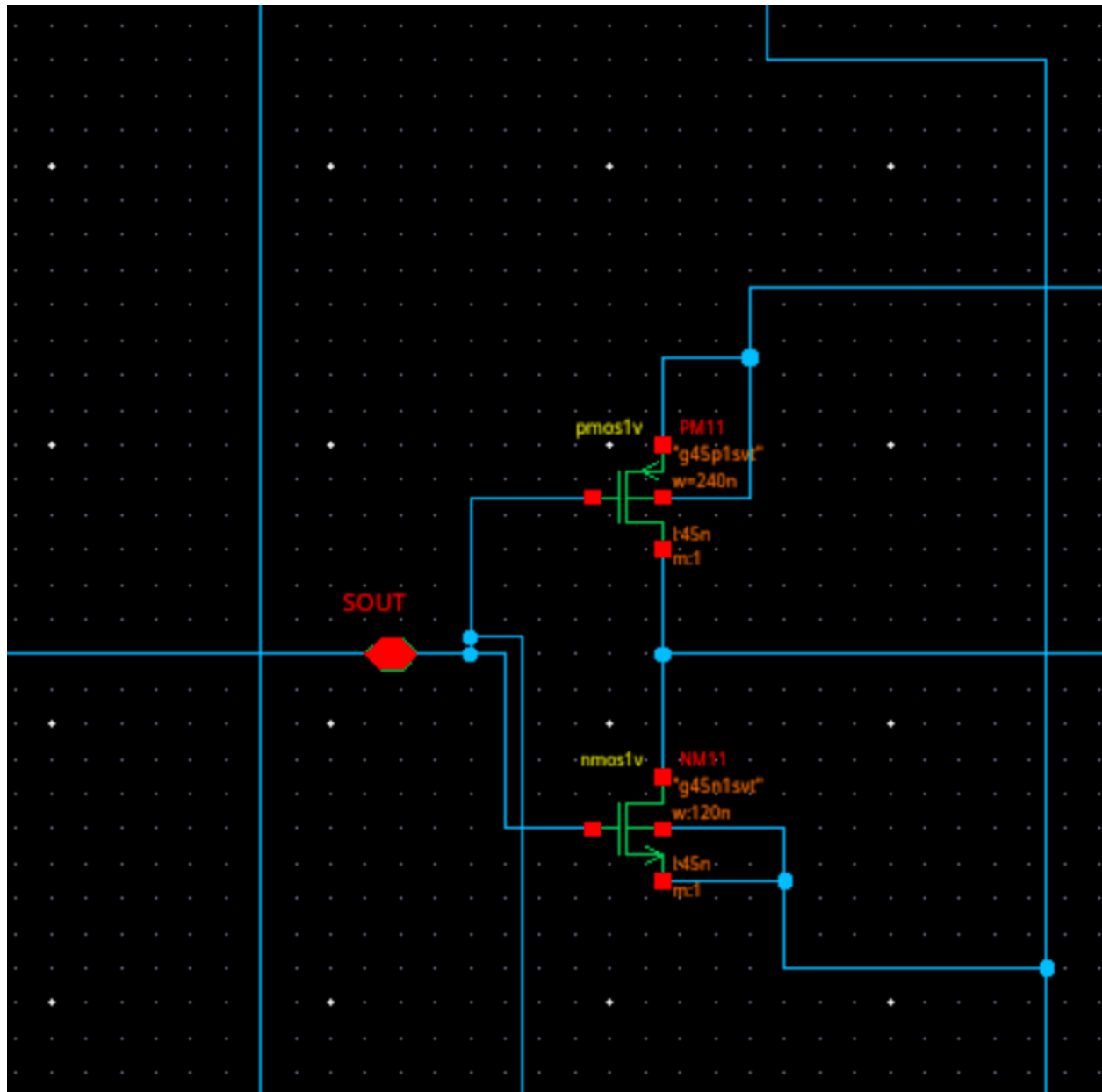


NOT GATE

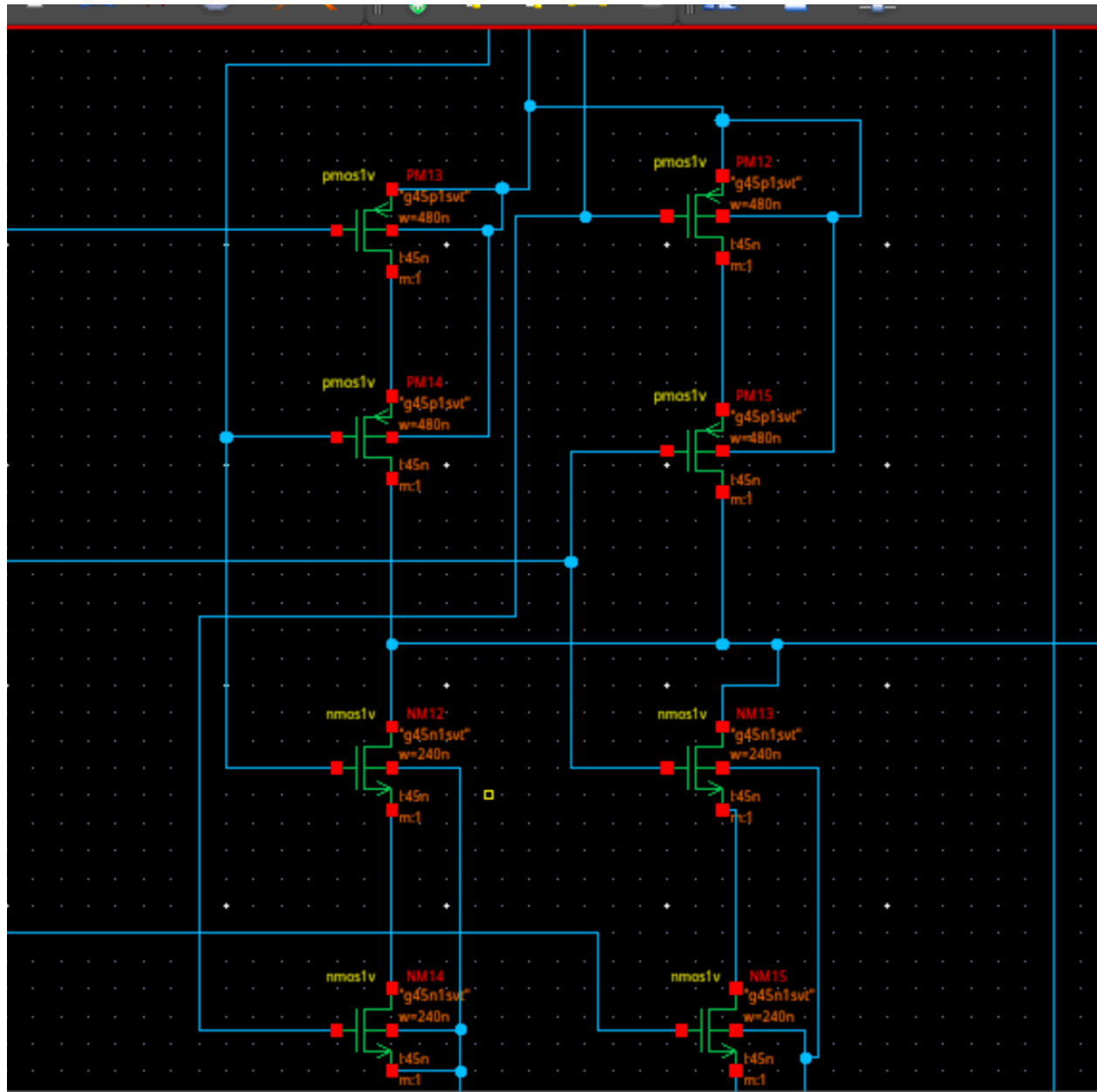


XOR gate

 


NAND gate

 

NOR GATE

 


Latches

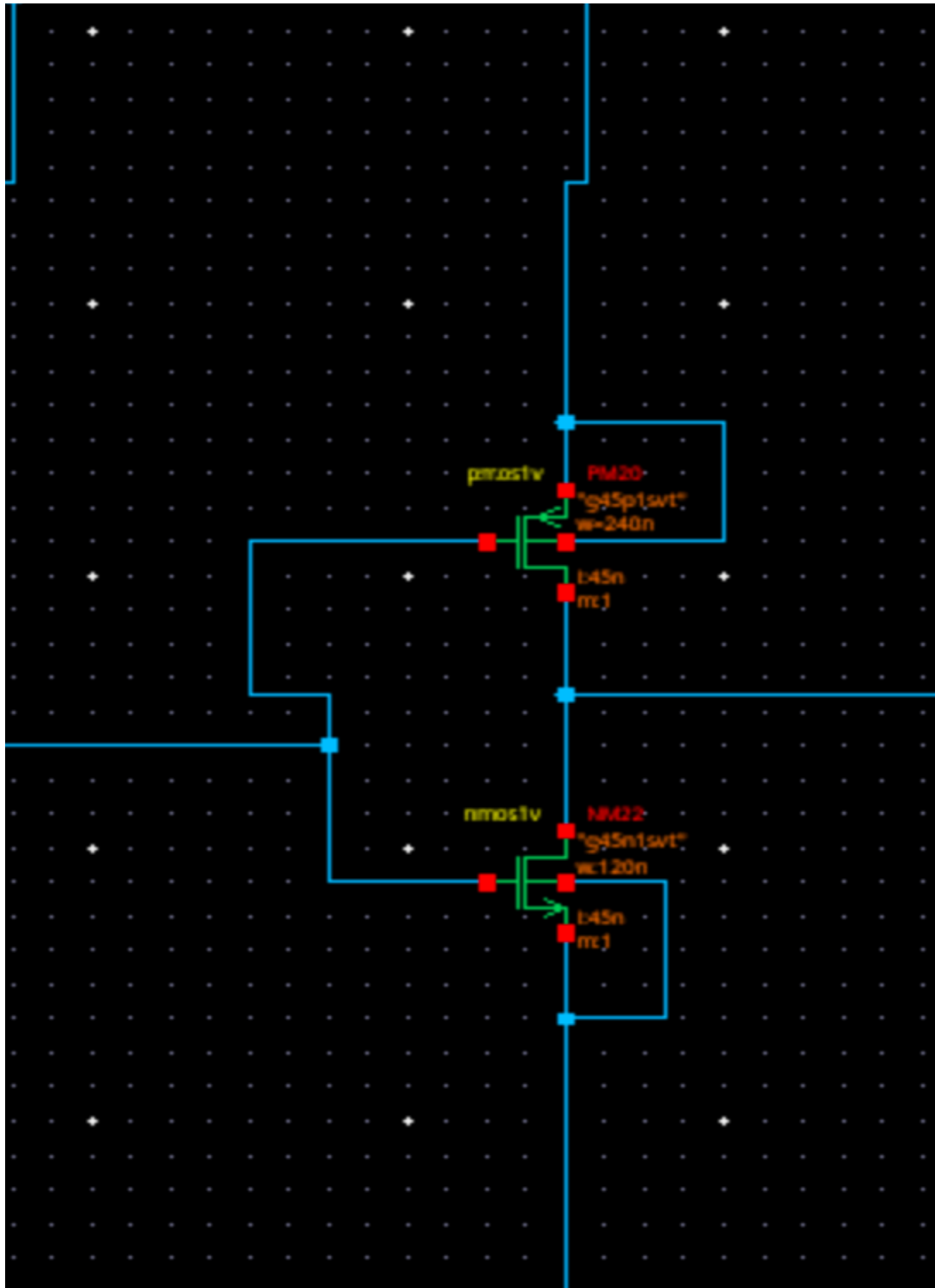


LAST inverter

3.1 Solution

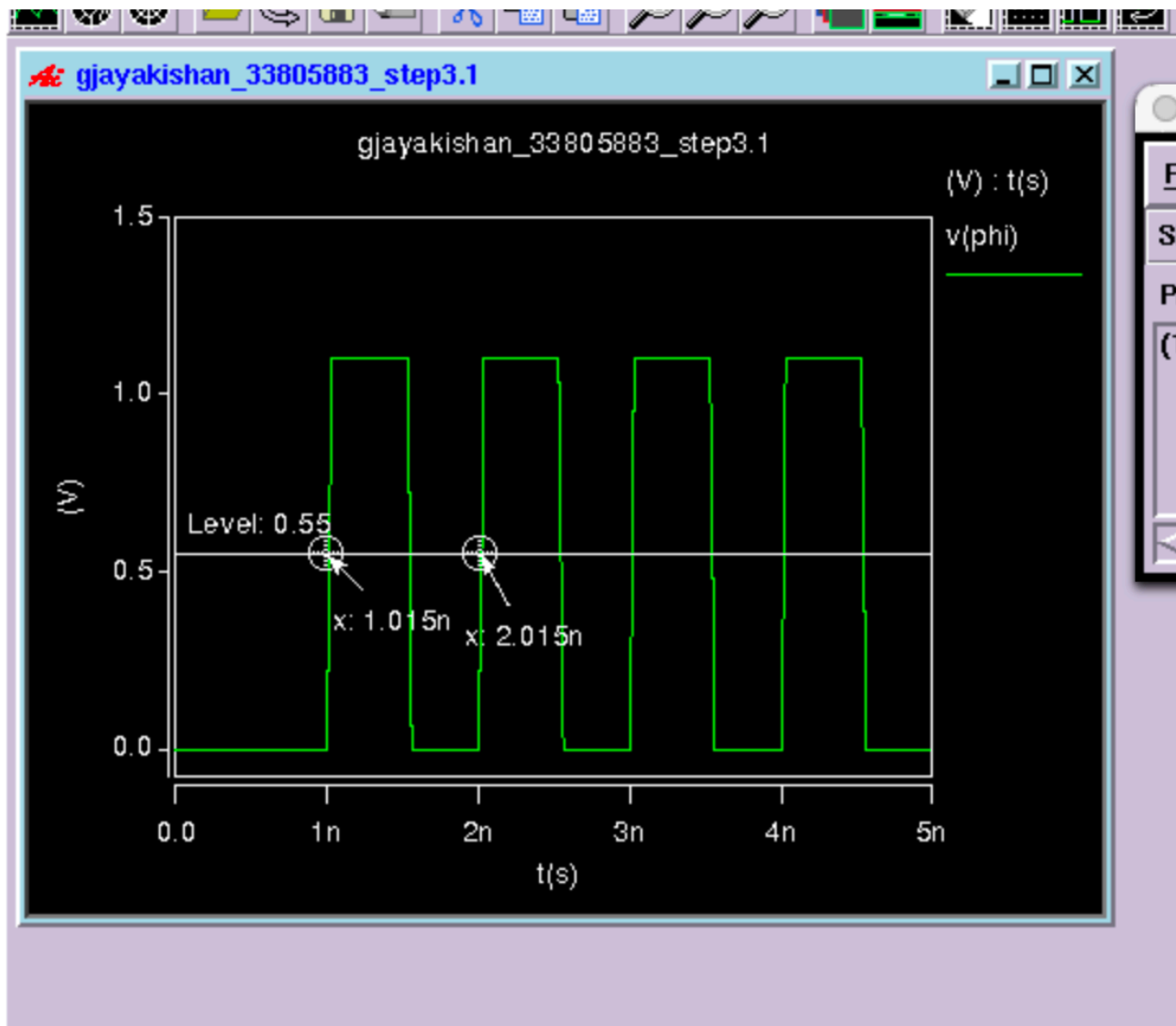


Measured 50% crossing of PHI at 1.015 ns (first rising edge) and 2.015 ns (second rising edge), matching theoretical values for $t_{clk} = 1$ ns, $t_r = 30$ ps

3.2 Solution

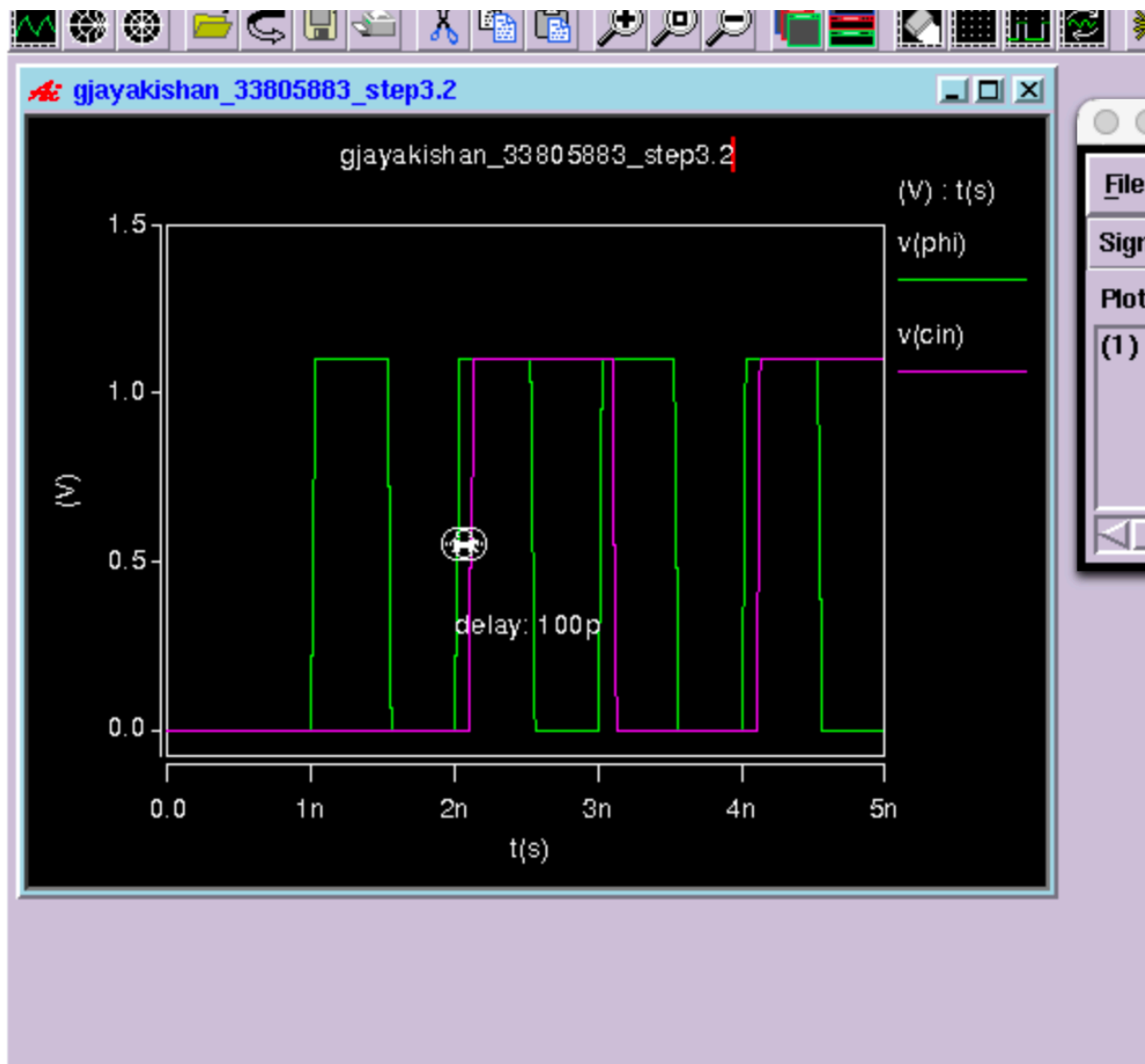


3.3 Solution


giavakishan_33805883_step3.3

 


Step 4.1 solution

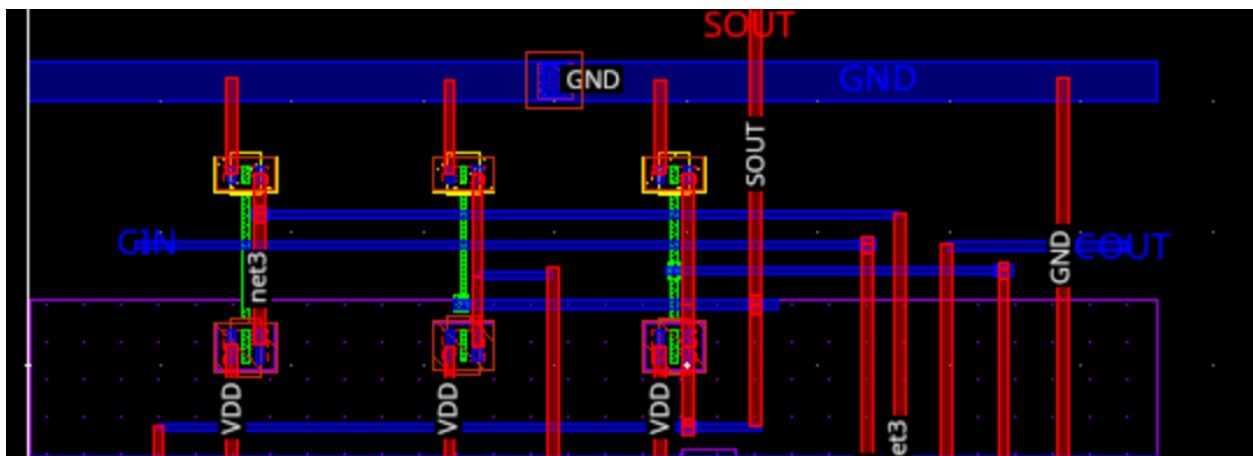


4.2 solution

 

Step 4.3

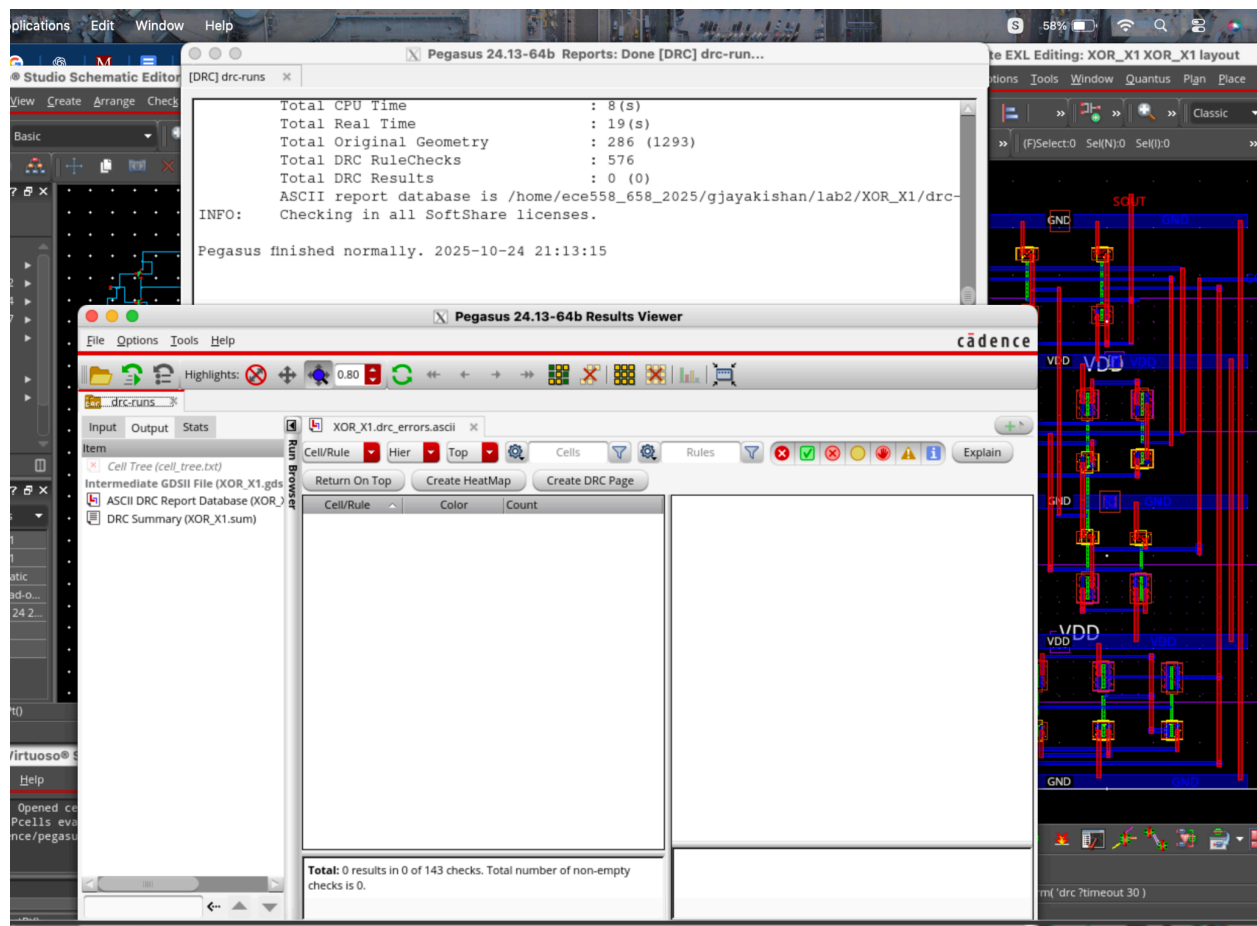

4.4 solution

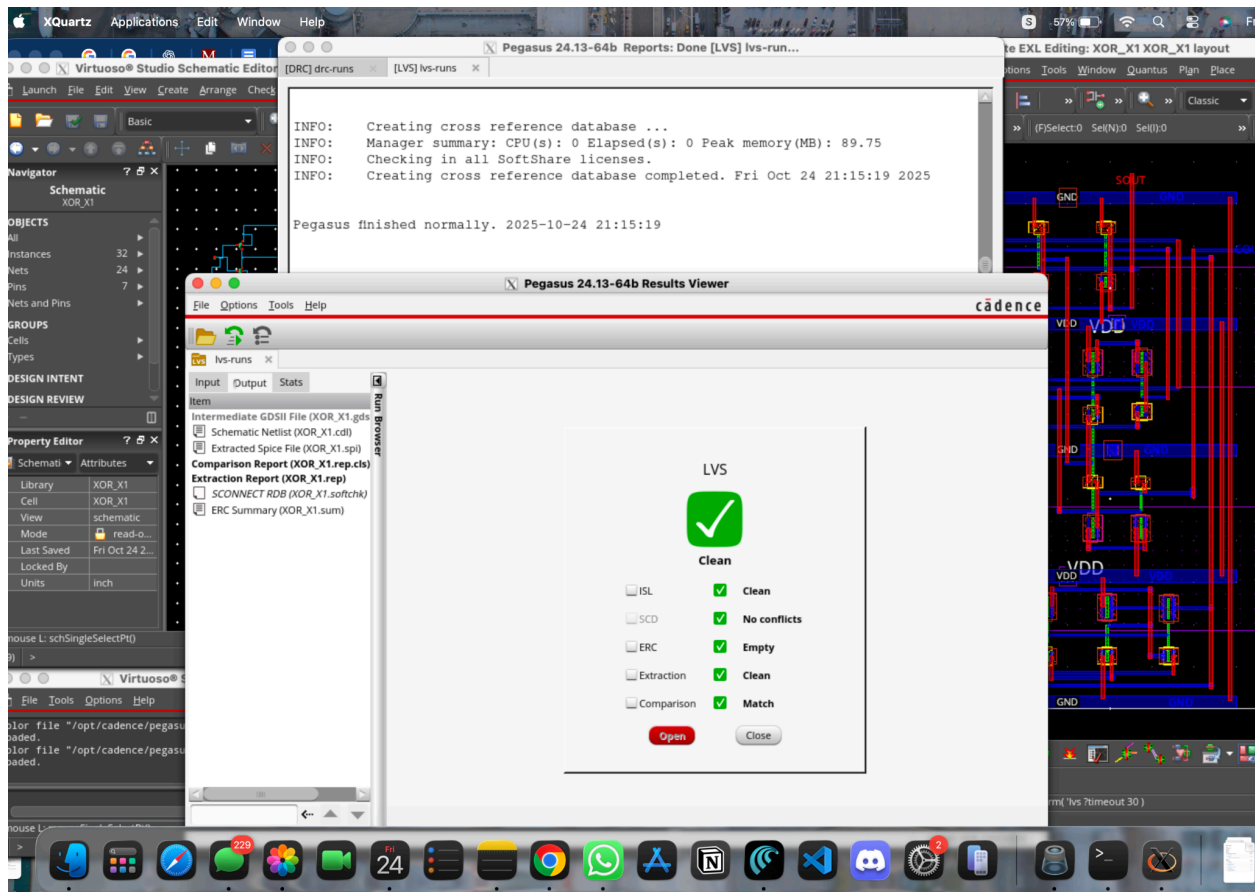

4.5 solution

The measured average powers were 1.064×10^{-5} W at 500 MHz, 1.419×10^{-5} W at 667 MHz, 2.112×10^{-5} W at 1 GHz, and 4.187×10^{-5} W at 2 GHz. The results show a nearly linear increase in power with frequency, indicating that dynamic switching power dominates total consumption in this CMOS design.

5.2 solution

The total power of the circuit can be modeled as a linear function of frequency:

$$P(f) = P_{\text{static}} + k f$$

where P_{static} represents the leakage (static) power and k is the dynamic power coefficient. Using the 500 MHz and 2 GHz results,

$$k = (P_2 - P_1) / (f_2 - f_1) = (4.187 \times 10^{-5} - 1.064 \times 10^{-5}) / (2.0 \times 10^9 - 5.0 \times 10^8) = 2.08 \times 10^{-14} \text{ W/Hz}.$$

The static power was then obtained as

$$P_{\text{static}} = P_1 - k f_1 = 1.064 \times 10^{-5} - (2.08 \times 10^{-14})(5.0 \times 10^8) = 2.3 \times 10^{-7} \text{ W}.$$

Thus, the fitted power-frequency equation becomes

$$P(f) = 2.3 \times 10^{-7} + (2.08 \times 10^{-14}) f.$$

The slope k represents the dynamic switching component of power, while the intercept corresponds to static leakage power of about 0.23 μW . The model fits the measured data almost perfectly, confirming the expected linear relationship between power and frequency in CMOS logic.

5.3 solution

The frequency at which static power equals ten percent of the total power can be found from the relationship

$$P_{\text{static}} = 0.1 (P_{\text{static}} + k f),$$

which simplifies to $f = 9 P_{\text{static}} / k$. Substituting the calculated values gives

$$f = 9 (2.3 \times 10^{-7}) / (2.08 \times 10^{-14}) = 9.9 \times 10^7 \text{ Hz} \approx 100 \text{ MHz}.$$

At approximately 100 MHz, static leakage power contributes about ten percent of the total power. Beyond this frequency, dynamic switching power overwhelmingly


dominates, which is consistent with the expected behavior of a 45 nm CMOS circuit operating at nominal voltage.

In summary, the post-layout power analysis of the XOR_X1 cell demonstrates a clear linear scaling of average power with clock frequency. The static power is about 2.3×10^{-7} W, the dynamic coefficient k is 2.08×10^{-14} W/Hz, and the crossover frequency where static power contributes ten percent of total power is around 100 MHz. At higher frequencies, total power is almost entirely dynamic, confirming typical CMOS operation.

6.1 solution


To check for hold-time failures, I varied the timing of the RST signal relative to the rising edge of the clock (PHI). Using the extracted netlist, RST was defined as a PWL source so its rising edge could be shifted earlier or later. When RST rose too soon, the stored output (SOUT) changed one cycle early, indicating a hold-time violation. I measured the timing offset between RST and PHI (50 % point) using an HSPICE `.meas` command

6.2 solution

 

When RST rose 20 ps before PHI ($\Delta t = -20$ ps), SOUT went high one cycle too early, showing a clear hold-time failure. The waveform confirms this: the RST (purple) edge precedes PHI (green), and SOUT (cyan) switches prematurely. The measured offset of -20 ps marks the violation.

Solution 6.3

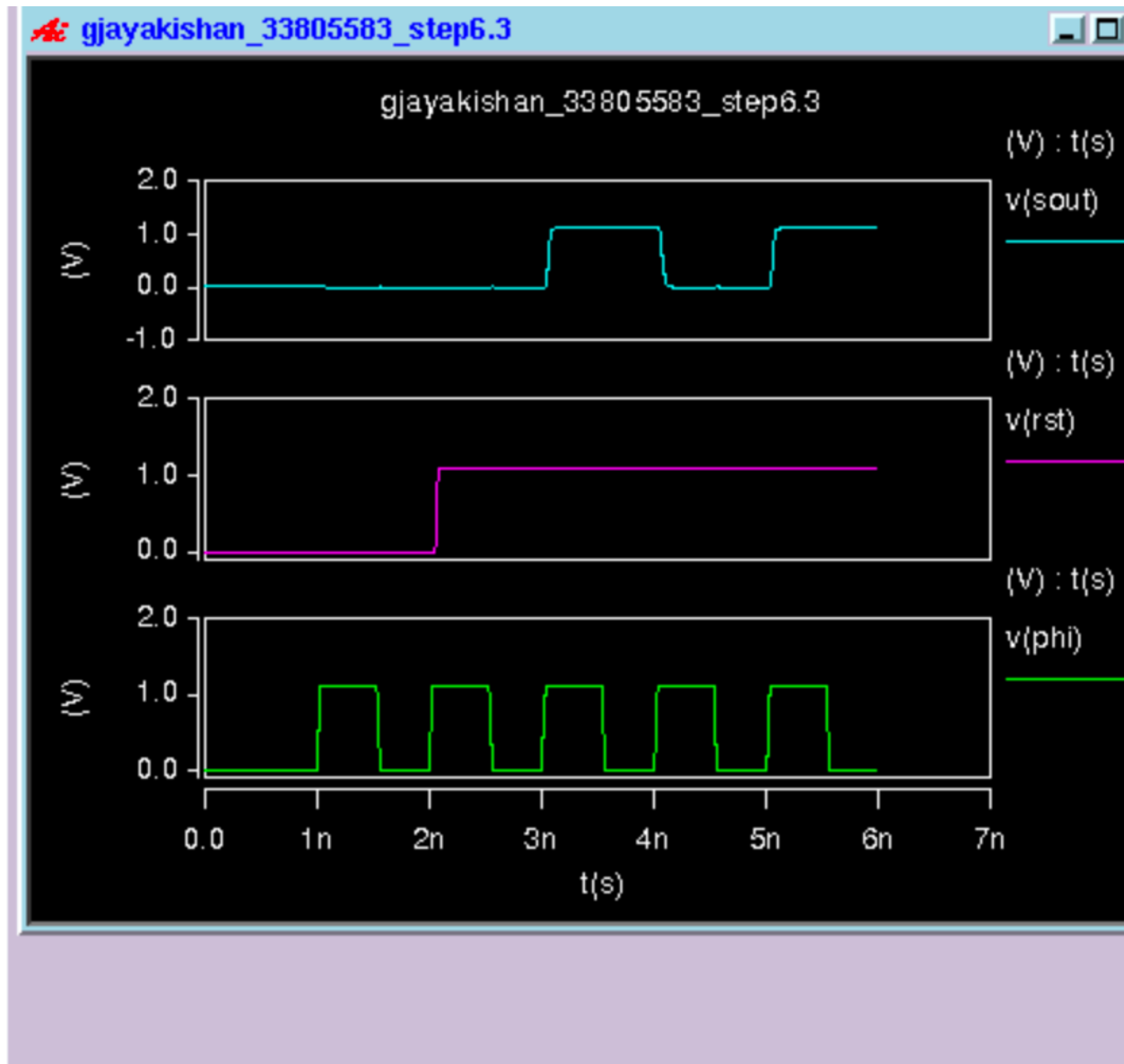

Delaying RST by +10 ps relative to PHI removes the failure. RST now rises slightly after PHI, and SOUT stays stable until the next valid cycle. The waveform shows normal behavior: no premature switching and correct data storage.

